

# SOLUTIONS MANUAL

## ESSENTIALS OF ELECTRICAL AND COMPUTER ENGINEERING

DAVID V. KERNS, JR. • J. DAVID IRWIN



Upper Saddle River, New Jersey 07458

Associate Editor: *Alice Dworkin*  
Supplements Editor: *Carole Snyder*  
Executive Managing Editor: *Vince O'Brien*  
Managing Editor: *David A. George*  
Production Editor: *Barbara A. Till*  
Supplement Cover Manager: *Daniel Sandin*  
Manufacturing Buyer: *Ilene Kahn*



© 2004 by Pearson Education, Inc.  
Pearson Prentice Hall  
Pearson Education, Inc.  
Upper Saddle River, NJ 07458

All rights reserved. No part of this book may be reproduced in any form or by any means, without permission in writing from the publisher.

The author and publisher of this book have used their best efforts in preparing this book. These efforts include the development, research, and testing of the theories and programs to determine their effectiveness. The author and publisher make no warranty of any kind, expressed or implied, with regard to these programs or the documentation contained in this book. The author and publisher shall not be liable in any event for incidental or consequential damages in connection with, or arising out of, the furnishing, performance, or use of these programs.

Pearson Prentice Hall® is a trademark of Pearson Education, Inc.

This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

**ISBN 0-13-047841-5**

Pearson Education Ltd., *London*  
Pearson Education Australia Pty. Ltd., *Sydney*  
Pearson Education Singapore, Pte. Ltd.  
Pearson Education North Asia Ltd., *Hong Kong*  
Pearson Education Canada, Inc., *Toronto*  
Pearson Educación de México, S.A. de C.V.  
Pearson Education—Japan, *Tokyo*  
Pearson Education Malaysia, Pte. Ltd.  
Pearson Education, Inc., *Upper Saddle River, New Jersey*

# Contents

1	Introduction	1
2	DC Circuits	5
3	Transient Analysis	36
4	AC Steady-State Analysis	73
5	Steady-State Power Analysis	118
6	Magnetically Coupled Circuits and Transformers	149
7	Network Frequency Characteristics	168
8	Introduction to Electronics	192
9	Operational Amplifiers (Op Amps)	200
10	Semiconductors, Diodes, and Power Supplies	212
11	Transistor Fundamentals: Switches, Large-Signal Amplifiers, and Power Electronics	229
12	Small-Signal Transistor Amplifiers	247
13	Digital Logic Circuits	261
14	Digital Electronic Logic Gates	294
15	DC Machines	305
16	AC Polyphase Machines	316



## CHAPTER 1 H.W. SOLUTIONS

$$1.1 \quad F = k \frac{q_1 q_2}{d^2} \Rightarrow q_1 = \frac{F d^2}{k q_2} = \frac{(3 \times 10^{-3})(10^{-3} \text{ m})^2}{(8.99 \times 10^9)(1.6 \times 10^{-6})} = 2.09 \times 10^{-13} \text{ C.}$$

$$1.2 \quad F = k \frac{q_1 q_2}{d^2} = (8.99 \times 10^9) \frac{(6.5 \times 10^{-12} \text{ C})^2}{(4 \times 10^{-6})^2} = 2.37 \times 10^{-2} \text{ N}$$

$$1.3 \quad F = k \frac{q_1 q_2}{d^2} = (8.99 \times 10^9) \frac{(0.03 \times 10^{-6})^2}{(10^{-2})^2} = 8.09 \times 10^{-2} \text{ N. — Repulsive}$$

$$1.4 \quad F = k \frac{q_1 q_2}{d^2} = (8.99 \times 10^9) \frac{(1.6 \times 10^{-19})^2}{[(5.3 \times 10^{-9})(10^{-2})]^2} = 8.19 \times 10^{-8} \text{ N}$$

1.5 To solve problems of this type, first use the "like or unlike" charge rule to determine the direction of the force; then use Eq 1.1 to determine the magnitude

a)  $q_1 = -2 \text{ mC}; q_2 = 4 \text{ mC}; q_3 = 10 \text{ mC}$

$$F_{q_1} = k \frac{q_1 q_2}{d_{12}^2} + k \frac{q_1 q_3}{d_{13}^2} \quad \text{where} \quad d_{12} = 5 \text{ cm} = 0.05 \text{ m}$$

Both  $q_2$  &  $q_3$  attract  $q_1$  to the right.

$$F_{q_1} = (8.99 \times 10^9)(2 \times 10^{-3}) \left[ \frac{4 \times 10^{-3}}{(0.05)^2} + \frac{10 \times 10^{-3}}{(0.15)^2} \right]$$

$$F_{q_1} = 1.28 \times 10^7 \text{ N}$$

The force on  $q_2$  caused by  $q_1$  is to the left; The force on  $q_2$  caused by  $q_3$  is also to the left. Therefore total force is the sum, and directed to the left

$$F_{q_2} = k \frac{q_2 q_1}{d_{12}^2} + k \frac{q_2 q_3}{d_{23}^2} \quad \text{where} \quad d_{12} = 0.05 \text{ m}$$

$$d_{23} = 0.10 \text{ m}$$

$$F_{q_2} = (8.99 \times 10^9) \left[ \frac{(4 \text{ mC})(2 \text{ mC})}{0.05^2} + \frac{(4 \text{ mC})(10 \text{ mC})}{0.10^2} \right]$$


$$F_{q_2} = (8.99 \times 10^9) [3.2 \times 10^{-3} + 4.0 \times 10^{-3}] = 6.47 \times 10^7 \text{ N}$$

The force on  $q_3$  caused by  $q_1$  is to the left; the force on  $q_3$  caused by  $q_2$  is to the right. Therefore if we let the right be defined as the "+" direction:

$$F_{q_3} = -k \frac{q_3 q_1}{d_{13}^2} + k \frac{q_3 q_2}{d_{23}^2}$$

$$= (8.99 \times 10^9) \left[ \frac{(10 \text{ mC})(2 \text{ mC})}{0.15^2} + \frac{(10 \text{ mC})(4 \text{ mC})}{0.10^2} \right]$$
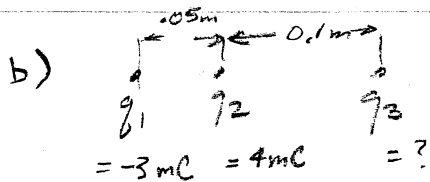
$$= (8.99 \times 10^9) [8.89 \times 10^{-4} + 4 \times 10^{-3}] = 4.40 \times 10^7 \text{ N}$$



Assume the right is "+" direction

$$F_{q_2} (\text{from } q_1) = -k \frac{q_2 q_1}{d_{12}^2} \\ = -(8.99 \times 10^9) \frac{(4\text{mC})(3\text{mC})}{(0.05)^2} \\ = -4.315 \times 10^7 \text{ N}$$

For the total force on  $q_2$  to be zero,  $q_3$  must create an equal and opposite force on  $q_2$ . Since  $q_2$  is "+"  $q_3$  must be "-" to create attractive force to the right.

$$F_{q_2} (\text{from } q_3) = 4.315 \times 10^7 \text{ N} = k \frac{(4\text{mC})(q_3)}{(0.1)^2} \\ q_3 = - \frac{(4.315 \times 10^7)(0.1)^2}{k (4\text{mC})} = -1.2 \times 10^{-2} \text{ C}$$

1.6 insulators: glass, rubber, ceramics, plastic, wood (dry)  
conductors: iron, gold, salt water, silver, brass, copper

1.7 a) wet aluminium   b) salt water   c) copper

1.8  $i = \frac{\Delta q}{\Delta t} = \frac{(8.2 \times 10^{21})(1.6 \times 10^{-19})}{10} = 131 \text{ A}$

1.9  $\Delta q = i \Delta t = (120)(6) = 720 \text{ C}$   
# electrons =  $\frac{720 \text{ C}}{1.6 \times 10^{-19} \text{ C/e}} = 4.5 \times 10^{21}$  electrons

1.10  $i = \frac{\Delta q}{\Delta t} = \frac{(3 \times 10^{19})(1.6 \times 10^{-19})}{5} = 0.96 \text{ A}$

1.11  $3\text{A} - 1\text{A} = 2\text{A}$  (away from the node)

1.12  $I_H = \frac{I_T}{2} = \frac{6.5}{2} = 3.25 \text{ A}$

1.13  $i = 0.2 \text{ A} = \frac{\Delta q}{\Delta t} \Rightarrow \text{if } \Delta t = 1 \quad \Delta q = 0.2 \text{ C}$   
# electrons =  $\frac{\Delta q}{q} = \frac{0.2 \text{ C}}{1.6 \times 10^{-19}} = 1.25 \times 10^{18}$  electrons

1.14 a)  $150 \cdot 10^3 \text{ A}$    b)  $2 \cdot 20 \text{ A}$    c)  $10^4 \text{ A}$    d)  $10^{-8} \text{ A}$

1.15  $V = \frac{dW}{dq} = \frac{\Delta W}{\Delta q} = \frac{3}{0.25} = 12 \text{ V}$

1.16 a)  $I = 0.5 \text{ A}$    # electrons/sec =  $\frac{0.5}{1.6 \times 10^{-19}} = 3.125 \times 10^{18} \text{ e/sec}$

# sec in half hour =  $60 \times 30 = 1800$

$\therefore$  # electrons in half-hour =  $(1800)(3.125 \times 10^{18}) = 5.625 \times 10^{21}$

$$b) P = VI = 12(0.5) = 6 \text{ W.}$$

$$c) E = P \Delta t = \left[ 6 \frac{\text{Joules}}{\text{sec}} \right] [1800 \text{ sec}] = 1.08 \times 10^4 \text{ J.}$$

$$1.17 \quad W = Vq = (25 \times 10^3)(1.6 \times 10^{-19}) = 4 \times 10^{-15} \text{ J}$$

$$1.18 \quad W = Vq = (1)(1.6 \times 10^{-19}) = 1.6 \times 10^{-19} \text{ J}$$

$$1.19 \quad \Delta W = V \Delta q$$

$$\Delta q = i \Delta t = (150)(1) = 150 \text{ C}$$

$$\Delta W = 12(150) = 1800 \text{ J.}$$

$$1.20 \quad 1) \text{ dc} \quad 2) \text{ dc} \quad 3) \text{ ac} \quad 4) \text{ dc} \quad 5) \text{ ac} \quad 6) \text{ dc}$$


$$1.21 \quad 1) 10^{14} \text{ Hz} \quad 2) 10^7 \text{ Hz} \quad 3) 10^{21} \text{ Hz}$$

$$1.22 \quad a) 10^8 \text{ Hz} \quad b) 10^{16} \text{ Hz} \quad c) 10^{19} \text{ Hz}$$

$$1.23 \quad a) V = -15 \text{ V}; I = 1 \text{ A}$$

$$b) V = 2 \text{ V}; I = 2 \text{ A}$$

$$c) V = 1 \text{ V}; I = -1 \text{ A}$$

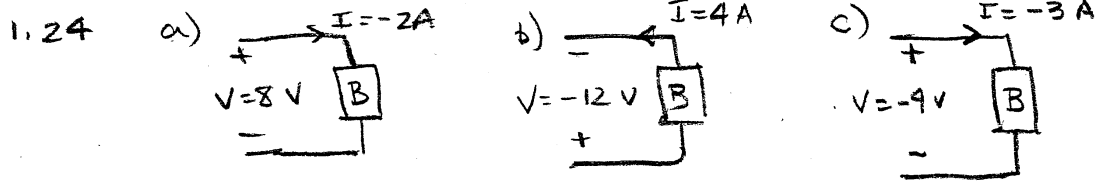

1.25

$$a) P = VI = (3)(2) = 6 \text{ W absorbing power}$$

(+ current enters + node)

$$b) P = (-10)(3) = 30 \text{ W - absorbing power}$$

(+ current enters + node)

$$c) P = VI = (6)(4) = 24 \text{ W - supplying power}$$

(+ current exits + node)

$$1.26 \quad a) \text{ A absorbing; } + \text{ current enters } + \text{ node}$$

$$\text{B supplying; } + \text{ current exits } + \text{ node}$$

$$P = VI = (3)(6) = 18 \text{ W (constant)}$$

$$E = P \cdot t = 18 \cdot t \quad t = \# \text{ secs/hr} = 60 \cdot 60 = 3600$$

$$E = (18)(3600) = 64,800 \text{ J}$$

$$b) \text{ A supplying; } + \text{ current exits } + \text{ node}$$

$$\text{B absorbing; } + \text{ current enters } + \text{ node}$$

$$P = VI = (6)(7) = 42 \text{ W}$$

$$E = P \cdot t = (42)(3600) = 151,200 \text{ J}$$

$$1.27 \quad a) \quad v_o = v_i \mu = (4.3)(25) = 107.5 \text{ V}$$

$$b) \quad v_o = v_i \mu = (30)(25) = 750 \text{ V}$$


$$1.28 \quad i_o = \beta i_i \Rightarrow i_i = \frac{i_o}{\beta} = \frac{2 \text{ mA}}{30} = 66.7 \mu\text{A}$$

$$1.29 \quad v_o = \mu v_i = (10^3)(3 \times 10^{-4}) = 0.30 \text{ V}$$

$$1.30 \quad v_o = \mu v_i = (48)(-3) = -144$$

$$1.31 \quad \mu = \frac{v_o}{v_i} = \frac{30}{6} = 5$$
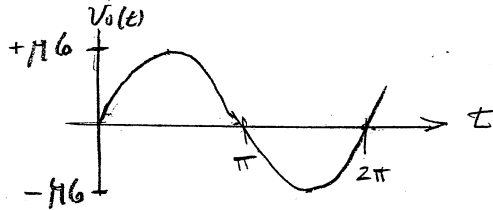
$$1.32 \quad v_o = \mu v_i = \mu 6 \sin t$$



$$1.33 \quad a) \quad i_o = i_R = g v_i = (10^{-3})(6) = 6 \text{ mA}$$

$$b) \quad i_o = i_R = g v_i = (10^{-3})(-9) = -9 \text{ mA}$$


$$1.34 \quad a) \quad i_o = i_R = \beta i_i = (25)(1 \text{ mA}) = 25 \text{ mA}$$

$$b) \quad i_o = i_R = \beta i_i = (25)(-6 \text{ mA}) = -150 \text{ mA} = -0.150 \text{ A}$$





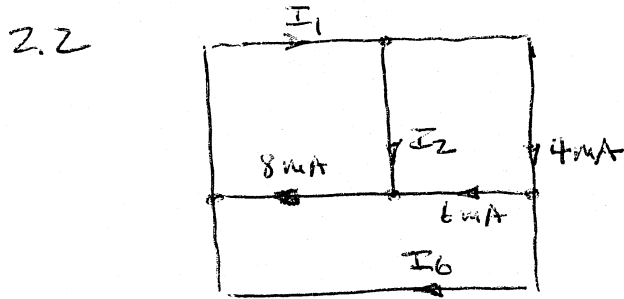
2.1  $10 = I_1 + 4 \Rightarrow I_1 = 6 \text{ mA}$



$$4 = 6 + I_6 \Rightarrow I_6 = -2 \text{ mA}$$

$$I_2 + 6 = 8 \Rightarrow I_2 = 2 \text{ mA}$$

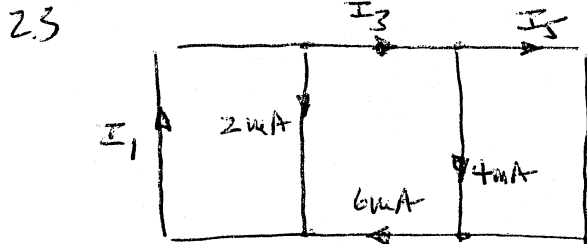
$$I_1 = I_2 + 4 \Rightarrow I_1 = 6 \text{ mA}$$



$$I_3 = 6 \text{ mA}$$

$$6 = I_1 + 2 \Rightarrow I_1 = 4 \text{ mA}$$
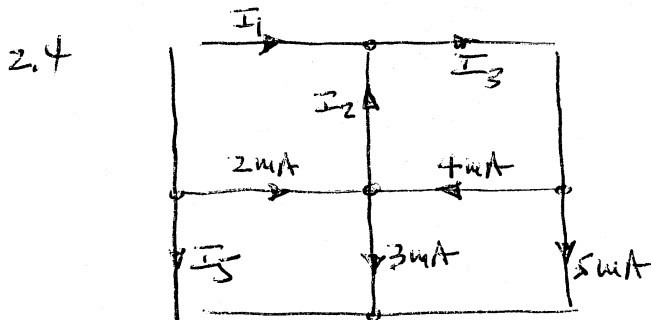
$$I_5 + 4 = 6 \Rightarrow I_5 = 2 \text{ mA}$$




$$I_3 = 4 + 5 \Rightarrow I_3 = 9 \text{ mA}$$

$$-I_2 + 2 + 4 \cdot 3 = 0 \Rightarrow I_2 = 3 \text{ mA}$$

$$I_5 + 3 + 5 = 0 \Rightarrow I_5 = -8 \text{ mA}$$
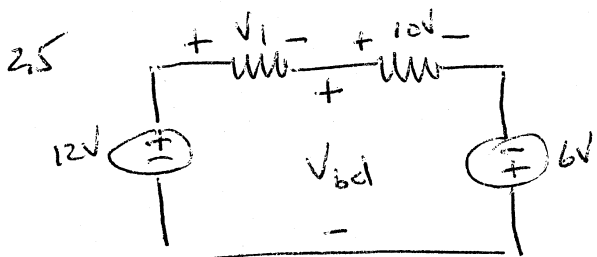
$$-I_1 - 2 + 8 = 0 \Rightarrow I_1 = 6 \text{ mA}$$




$$-12 + V_1 + 10 - 6 = 0$$

$$V_1 = 8 \text{ V}$$

$$-V_{bd} + 10 - 6 = 0$$

$$V_{bd} = 4 \text{ V}$$

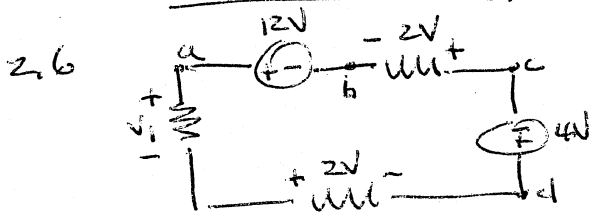

$$V_{bc} = -2 \text{ V}$$


$$-V_{da} + 4 + 2 - 12 = 0$$

$$V_{da} = -6 \text{ V}$$

$$-V_1 + 12 - 2 - 4 - 2 = 0$$

$$V_1 = 4 \text{ V}$$

2.7

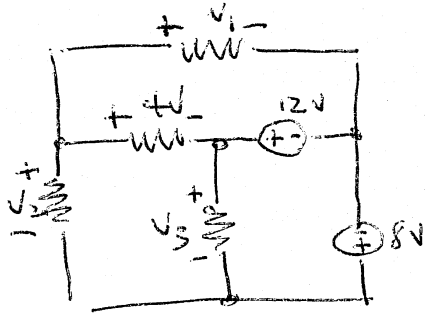


$$V_1 - 12 - 4 = 0 \Rightarrow V_1 = 16V$$

$$-V_3 + 12 - 8 = 0 \Rightarrow V_3 = 4V$$

$$-V_2 + 4 + V_3 = 0 \Rightarrow V_2 = 8V$$

2.8

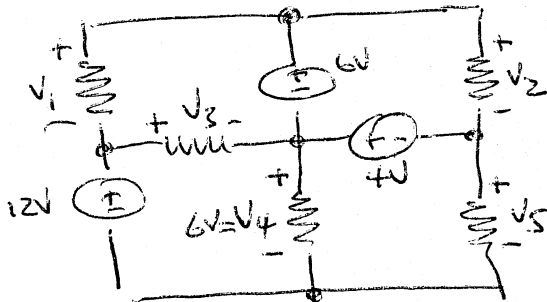

$$-6 + V_2 - 4 = 0 \Rightarrow V_2 = 10V$$

$$-6 + 4 + V_3 = 0 \Rightarrow V_3 = 2V$$

$$-12 + V_3 + 6 = 0 \Rightarrow V_3 = 6V$$


$$-V_1 + 6 - V_3 = 0 \Rightarrow V_1 = 0V$$

$$2.9 \quad I = \frac{6}{3k} = 2\mu A$$

$$2.10 \quad R = \frac{12}{2k} = 6k\Omega$$

$$2.11 \quad \frac{V_3^2}{2k} = \frac{8}{k} \Rightarrow V_3^2 = (2 \times 10^3)(8 \times 10^3) = 16 ; V_3 = \pm 4V$$


2.12

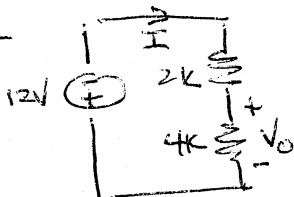

$$I = \frac{-12}{2k + 4k} = -2\mu A$$

$$V_0 = \left(\frac{2}{k}\right)(4k) = -8V$$

2.13

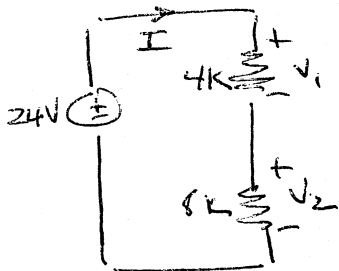


$$I = \frac{24}{4k + 8k} = 2\mu A$$

$$V_1 = 4kI = 8V$$

$$V_2 = 8kI = 16V$$


2.14

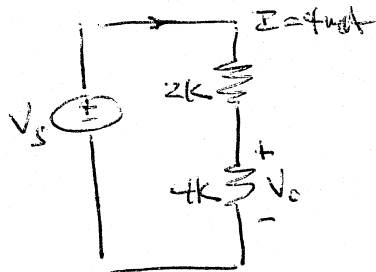

$$V_o = (4k) \left( \frac{4}{k} \right) = 16V$$

$$V_s = \frac{4}{k} (2k + 4k) = 24V$$


2.15

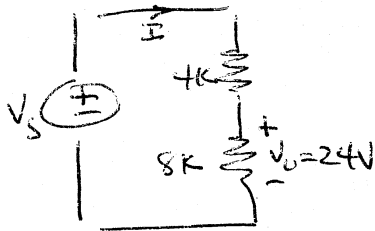

$$I = \frac{24}{8k} = 3mA$$

$$V_s = \frac{3}{k} (4k + 8k) = 36V$$

2.16

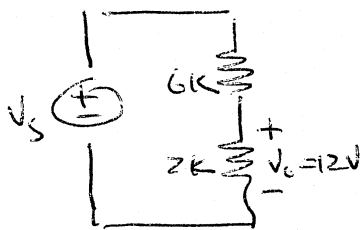


Voltage Div.

$$V_o = \frac{V_s (2k)}{6k + 2k} = 12$$


$$V_s = 48V$$

2.17

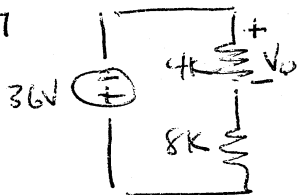


$$V_o = \frac{-36 (4k)}{4k + 8k} = -12V$$

2.18

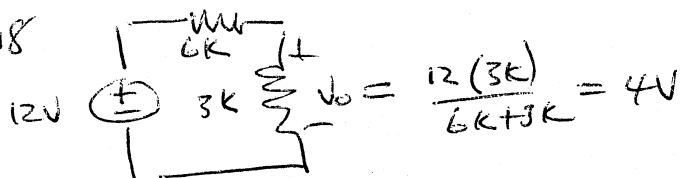


$$V_o = \frac{12 (3k)}{6k + 3k} = 4V$$

2.19

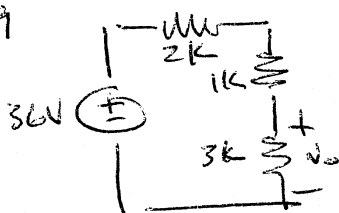

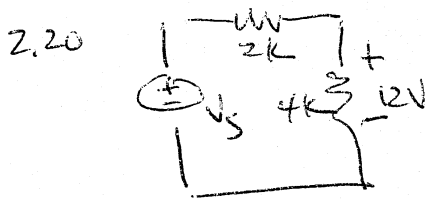
$$V_o = \frac{36 (3k)}{2k + 1k + 3k} = 18V$$




$$12 = \frac{V_s(4k)}{4k+2k}$$

$$V_s = 18V$$

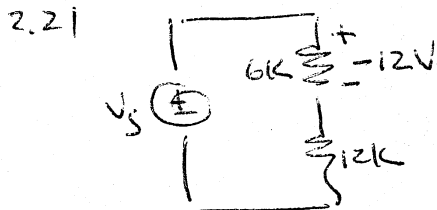


$$-12 = \frac{V_s(6k)}{6k+12k}$$

$$V_s = -36V$$

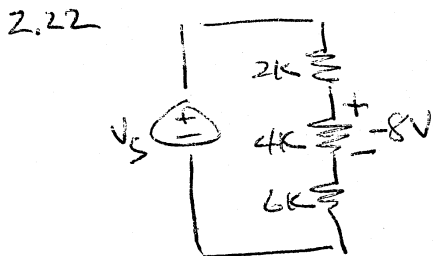


$$-8V = \frac{V_s(4k)}{2k+4k+6k}$$

$$V_s = -24V$$

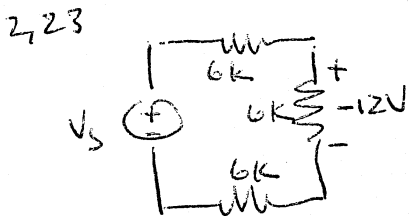


$$-12 = \frac{V_s(6k)}{(3)(6k)}$$

$$V_s = -36V$$

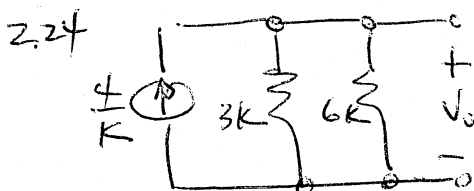


$$\frac{V_o}{3k} + \frac{V_o}{6k} = \frac{4}{K}$$

$$V_o = 8V$$

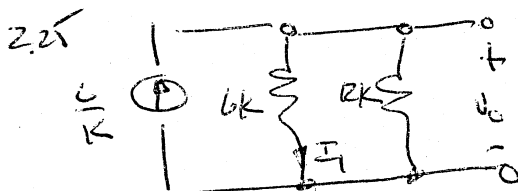


$$\frac{V_o}{6k} + \frac{V_o}{2k} = \frac{6}{K} \Rightarrow V_o = 24V$$

$$I_1 = \frac{24}{6k} = 4\mu A$$

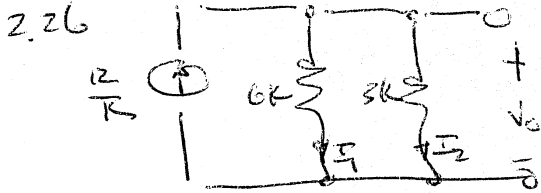


$$\frac{v_o}{6k} + \frac{v_o}{3k} = \frac{12}{k} \Rightarrow v_o = 24V$$
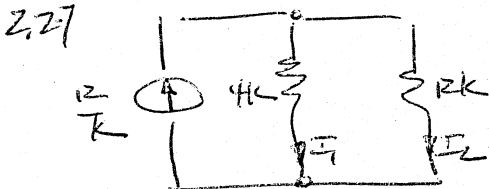
$$I_1 = \frac{24}{6k} = 4mA \quad I_2 = \frac{24}{3k} = 8mA$$




$$I_1 = \frac{12}{k} \left( \frac{2k}{4k+2k} \right) = 9mA$$

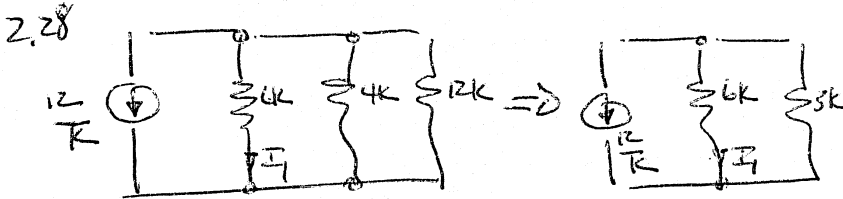
$$I_2 = \frac{12}{k} \left( \frac{4k}{4k+2k} \right) = 3mA$$


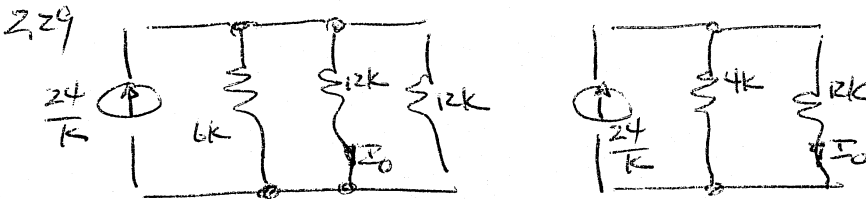
$$I_1 = \frac{-12/k (3k)}{3k+6k} = -4mA$$



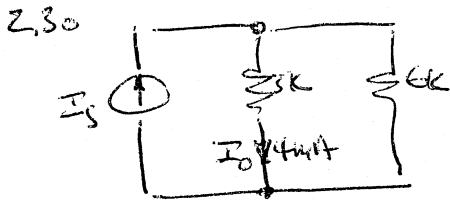
$$I_0 = \frac{24}{k} \left( \frac{4k}{4k+2k} \right) = 6mA$$




$$\frac{4}{k} = \frac{I_5 (6k)}{3k+6k}$$

$$I_5 = 6mA$$

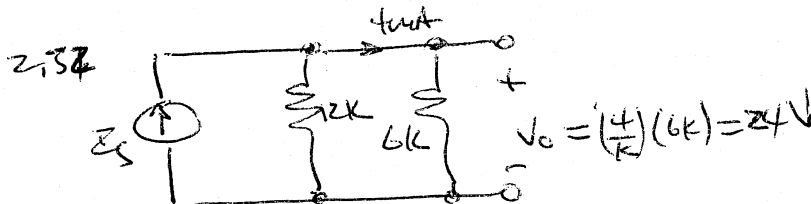

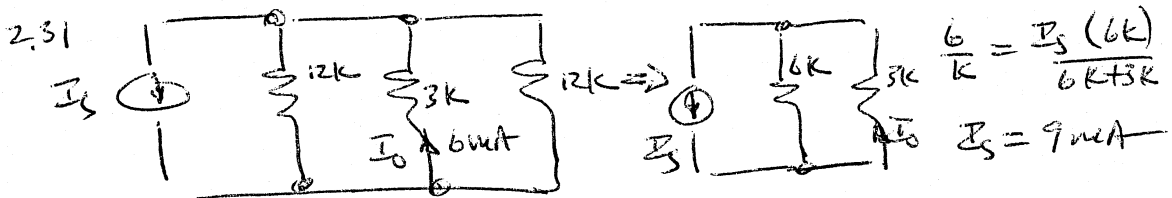
$$v_o = \left( \frac{4}{k} \right) (6k) = 24V$$



$$\frac{6}{k} = \frac{I_5 (6k)}{6k+3k}$$

$$I_5 = 9mA$$


2.33

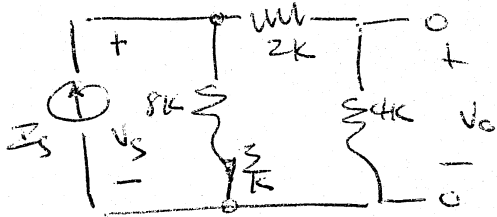

$$V_s = \left(\frac{3}{2}\right)(8k) = 24V$$

$$V_o = \frac{24(4k)}{2k+4k} = 16V$$

2.34


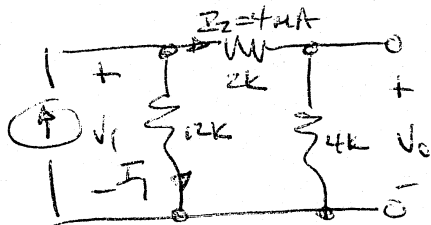


$$V_o = I_2(4k) = 16V$$

$$V_1 = I_2(2k+4k) = 24V$$


$$I_1 = \frac{24}{12k} = 2mA$$

2.35

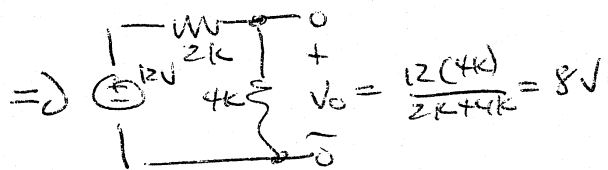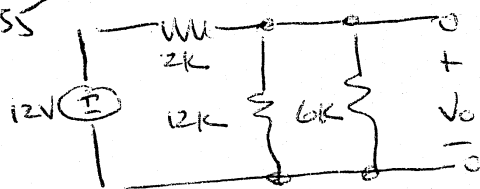

$$V_o = \frac{12(4k)}{2k+4k} = 8V$$

2.36

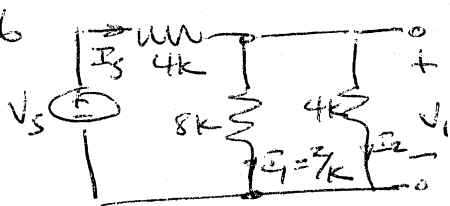


$$V_1 = 8k I_1 = 16V$$

$$I_2 = \frac{V_1}{4k} = 4mA$$

$$I_s = I_1 + I_2 = 6mA$$

$$V_o = 4k I_s + V_1 = 40V$$

2.37

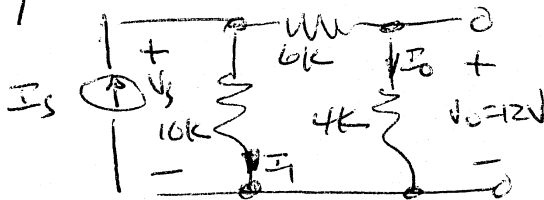



$$I_0 = \frac{12}{4k} = 3mA$$

$$V_s = I_0(4k+6k) = 30V$$






$$I_1 = \frac{V_s}{10k} = 3mA$$




$$I_s = I_1 + I_0 = 6mA$$

2.38

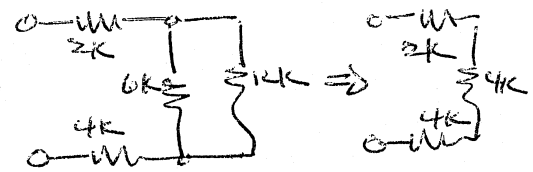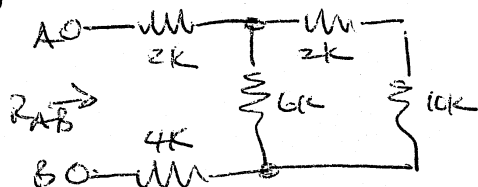

$$R_{AB} = 10k\Omega$$

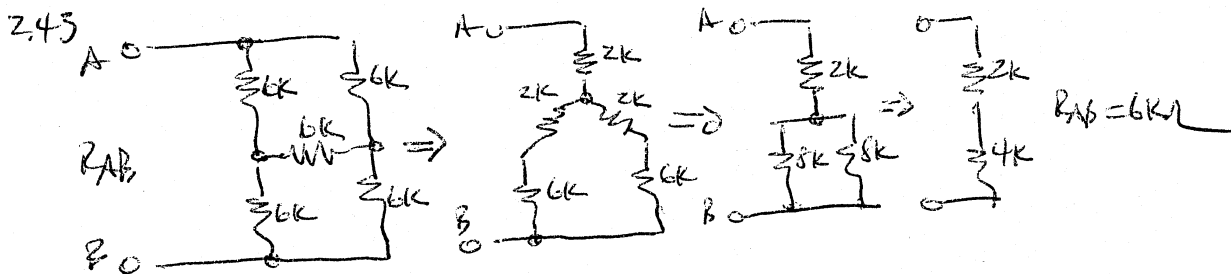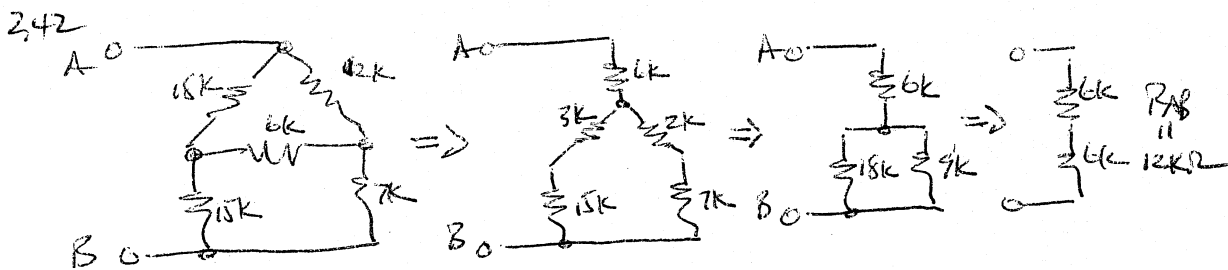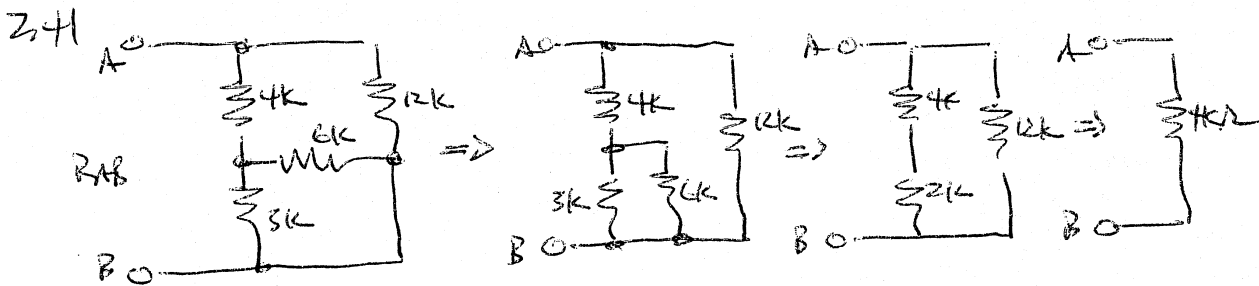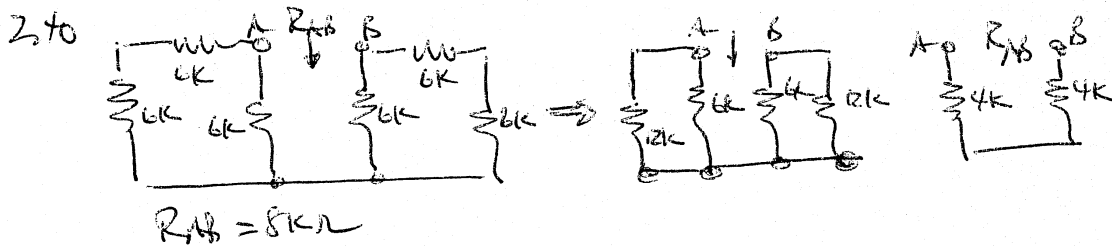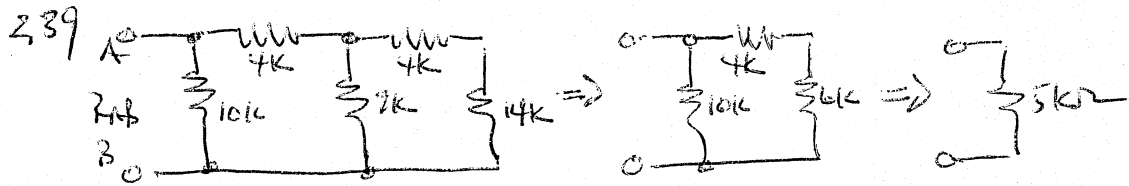

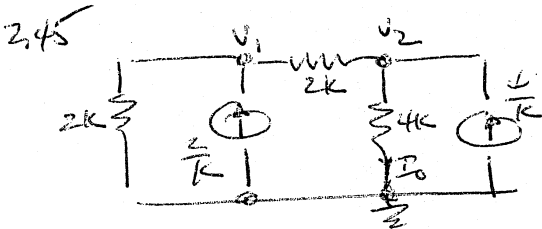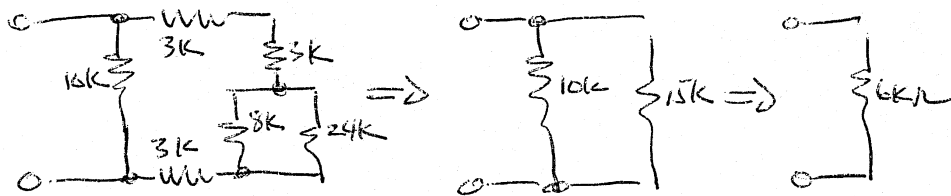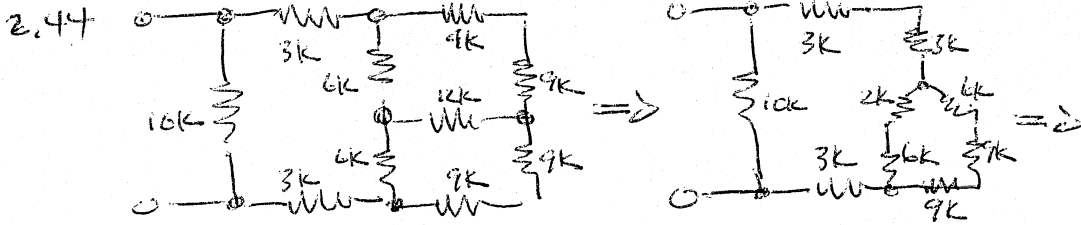

$$v_1 \left( \frac{1}{2k} + \frac{1}{2k} \right) - v_2 \left( \frac{1}{2k} \right) = \frac{2}{R}$$

$$-v_1 \left( \frac{1}{2k} \right) + v_2 \left( \frac{1}{2k} + \frac{1}{4k} \right) = \frac{4}{R}$$

$$v_1 - \frac{1}{2} v_2 = 2$$

$$-\frac{1}{2} v_1 + \frac{3}{4} v_2 = 4$$

$$\begin{bmatrix} 1 & -1/2 \\ -1/2 & 3/4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 4 \end{bmatrix}$$

$$\Delta = (1)(3/4) - (-1/2)(-1/2) = \frac{3}{4} - \frac{1}{4} = \frac{1}{2}$$



$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = 2 \begin{bmatrix} 3/4 & 1/2 \\ 1/2 & 1 \end{bmatrix} \begin{bmatrix} 2 \\ 4 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 \left( \frac{6}{4} + 2 \right) \\ 2 \left( 1 + 4 \right) \end{bmatrix} = \begin{bmatrix} 2 \left( 3\frac{1}{2} \right) \\ 2 \left( 5 \right) \end{bmatrix} = \begin{bmatrix} 7 \\ 10 \end{bmatrix}$$


$$I_0 = \frac{10}{4k} = 2.5 \text{ mA}$$



2.46

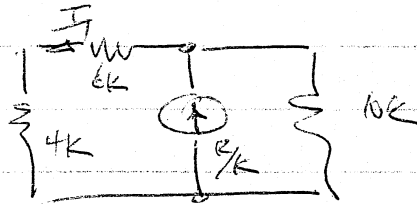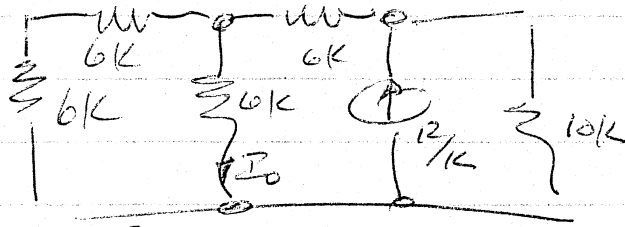


$$I_1 = \frac{2k}{2} = 1k$$

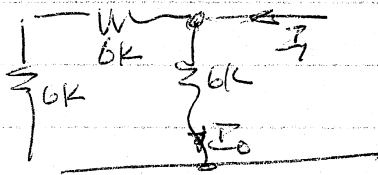

$$I_0 = \frac{I_1(2k)}{18k} = \frac{(1k)(2k)}{18k} = \frac{4}{9}A$$

2.47

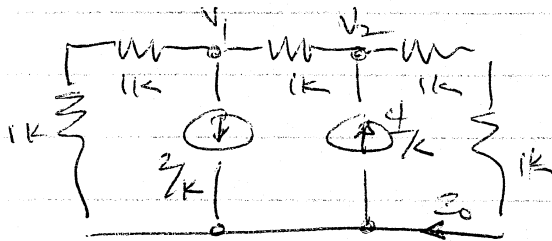

$$V_1 \left( \frac{1}{k} + \frac{1}{2k} + \frac{4}{5} \right) - V_2 \left( \frac{1}{k} \right) = -\frac{2}{k}$$

$$-V_1 \left( \frac{1}{k} \right) + V_2 \left( \frac{1}{k} + \frac{1}{2k} \right) = \frac{4}{k}$$

$$V_1 \left( \frac{3}{2} \right) - V_2 = -2$$

$$-V_1 + V_2 \left( \frac{3}{2} \right) = 4$$

$$V_1 = \frac{4}{5} \left[ -3 + 4 \right] = \frac{4}{5}$$


$$V_2 = \frac{4}{5} \left[ -2 + 6 \right] = \frac{16}{5}$$

$$\Delta = \frac{9}{4} - (-1)(-1) = \frac{9}{4} - \frac{1}{4} = \frac{8}{4} = 2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{4}{5} \begin{bmatrix} 3/2 & 1 \\ 1 & 3/2 \end{bmatrix} \begin{bmatrix} -2 \\ 4 \end{bmatrix}$$

$$\frac{2}{5} \begin{bmatrix} 10/5 & 12/5 \\ & & & \end{bmatrix}$$

2.48

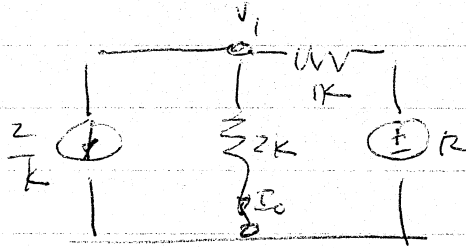

$$2 + \frac{v_1}{2k} + \frac{v_1 - 12}{1k} = 0$$


$$2 + \frac{v_1}{2} + \frac{v_1}{1} - 12 = 0$$

$$\frac{3}{2}v_1 = 10$$

$$v_1 = \frac{20}{3}V$$

$$I_0 = \frac{v_1}{2k} = \frac{10}{3k}A$$

2.49

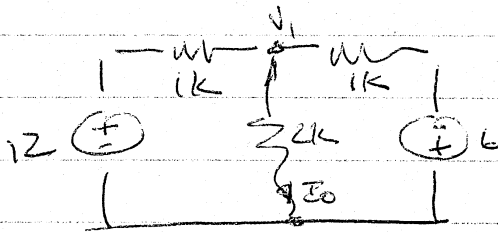

$$\frac{v_1 - 12}{1k} + \frac{v_1}{2k} + \frac{v_1 + 6}{1k} = 0$$


$$v_1 - 12 + \frac{v_1}{2} + v_1 + 6 = 0$$

$$\frac{5}{2}v_1 = 6$$

$$v_1 = \frac{12}{5}V$$

$$I_0 = \frac{v_1}{2k} = \frac{6}{5k}A$$

2.50

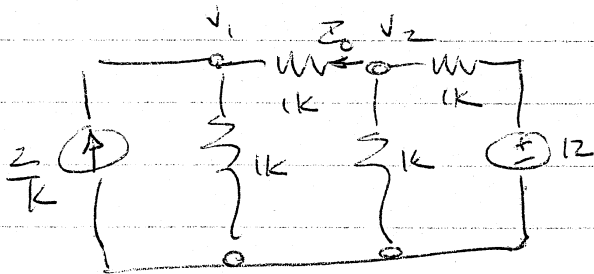

$$2v_1 - v_2 = 2$$

$$2\left(\frac{18}{5}\right) - v_2 = 2$$

$$\frac{36}{5} - 2 = v_2$$

$$\frac{36 - 10}{5} = v_2$$

$$\frac{26}{5} = v_2$$

$$v_1\left(\frac{1}{k} + \frac{1}{k}\right) - v_2\left(\frac{1}{k}\right) = \frac{2}{k}$$

$$-v_1\left(\frac{1}{k}\right) + v_2\left(\frac{1}{k} + \frac{1}{k} + \frac{1}{k}\right) = \frac{12}{k}$$

$$2v_1 - v_2 = 2$$


$$-v_1 + 3v_2 = 12$$


$$2v_1 - 2 = v_2$$

$$-v_1 + 3(2v_1 - 2) = 12$$

$$5v_1 - 6 = 12$$

$$v_1 = \frac{18}{5}V$$

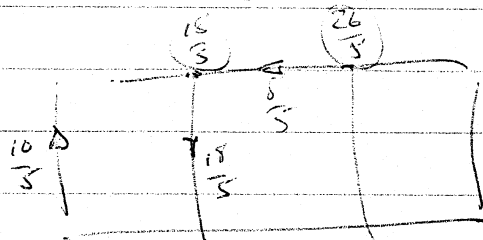

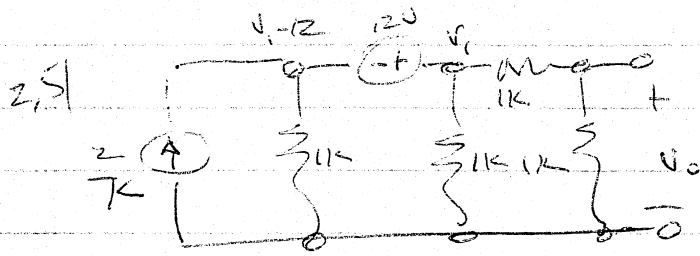


$$\frac{v_1 - 12}{1k} + \frac{v_1}{1k} + \frac{v_1}{2k} = \frac{2}{k}$$

$$v_1 + v_1 + \frac{v_1}{2} = 14$$

$$\frac{5}{2}v_1 = 14$$

$$v_1 = \frac{28}{5} \text{ V}$$
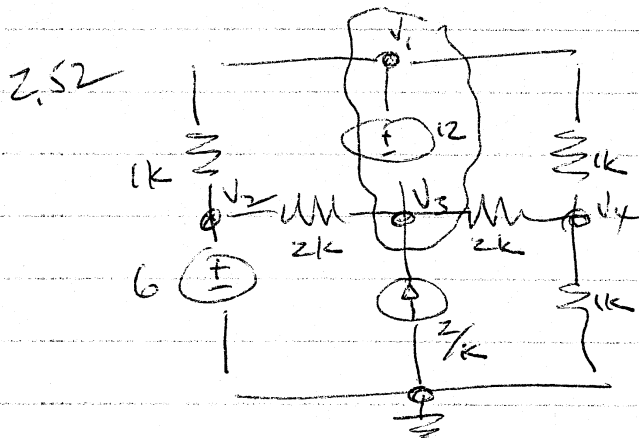
$$v_0 = \frac{1}{2}v_1 = \frac{14}{5} \text{ V}$$



$$\frac{v_1 - 6}{k} + \frac{v_3 - 6}{2k} + \frac{v_1 - v_4}{1k} + \frac{v_3 - v_4}{2k} = \frac{2}{k}$$

$$v_1 - v_3 = 12 \quad v_2 = 6$$

$$\frac{v_4 - v_3}{k} + \frac{v_4 - v_3}{2k} + \frac{v_4}{k} = 0$$

$$v_1 - 6 + \frac{v_3}{2} - 3 + v_1 - v_4 + \frac{v_3}{2} - \frac{v_4}{2} = 2$$

$$v_4 - v_1 + \frac{v_4}{2} - \frac{v_3}{2} + v_4 = 0$$

$$v_1 = v_3 + 12$$

$$v_3 + 12 + \frac{v_3}{2} - 3 + v_3 + 12 - v_4 + \frac{v_3}{2} - \frac{v_4}{2} = 2$$

$$v_4 - v_3 - 12 + \frac{v_4}{2} - \frac{v_3}{2} + v_4 = 0$$

$$3v_3 - \frac{3}{2}v_4 = -13$$

$$-\frac{3}{2}v_3 + \frac{5}{2}v_4 = 12$$


$$\Delta = (3)\left(\frac{5}{2}\right) - \left(-\frac{3}{2}\right)\left(-\frac{3}{2}\right) = \frac{15}{2} - \frac{9}{4} = \frac{21}{4}$$

$$\begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = \frac{4}{21} \begin{bmatrix} \frac{5}{2} & \frac{3}{2} \\ \frac{3}{2} & 3 \end{bmatrix} \begin{bmatrix} -13 \\ 12 \end{bmatrix}$$

$$v_3 = \frac{4}{21} \left( \frac{-65}{2} + \frac{36}{2} \right) = \left( \frac{4}{21} \right) \left( \frac{-29}{2} \right) = -\frac{58}{21} \text{ V}$$

$$v_4 = \frac{4}{21} \left( \frac{-39}{2} + \frac{72}{2} \right) = \left( \frac{4}{21} \right) \left( \frac{33}{2} \right)$$

$$= +\frac{66}{21} \text{ V}$$

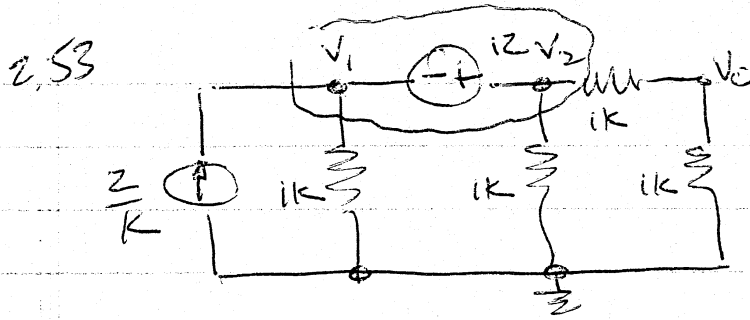

$$V_2 - V_1 = 12$$

$$-\frac{2}{K} + \frac{V_1}{1K} + \frac{V_2}{1K} + \frac{V_2 - V_0}{1K} = 0$$

$$\frac{V_0 - V_2}{1K} + \frac{V_0}{1K} = 0$$

$$-V_1 + V_2 = 12$$

$$V_1 + 2V_2 - V_0 = 2$$

$$-V_2 + 2V_0 = 0$$

$$\begin{bmatrix} -1 & 1 & 0 \\ 1 & 2 & -1 \\ 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_0 \end{bmatrix} = \begin{bmatrix} 12 \\ 2 \\ 0 \end{bmatrix}$$